

Frequency vs Current

Mark Schulist

2022-12-06

Capacitor

I expect that the current will be greater at higher frequencies since capacitors only pass signals, and there are more signals at higher frequencies.

The current increased with frequency. There is a directly proportional relationship between current and frequency with a capacitor.

$$X_c = \frac{1}{2\pi fC} \quad (1)$$

$$= \frac{[s]}{[F]} \quad (2)$$

$$= \frac{[s][V]}{[C]} \quad (3)$$


$$= \frac{[V]}{[A]} \quad (4)$$

There is an inverse relationship between capacitive reactance and frequency.

```
capacitor <- read_csv(here("EECS/frequency_vs_current/input/RLC-capacitor.csv"),
                      show_col_types = F)[1:201, ]
# Splitting the df into many dfs for every 3 columns
cap_dfs <- map(
  seq(1, ncol(capacitor), by = 3),
  ~ capacitor[, .x:(.x + 2)]
)
# Getting the frequency as a column
cap_df <- map_df(
  1:length(cap_dfs),
  ~ cap_dfs[[.x]] %>%
    mutate(frequency = parse_number(colnames(cap_dfs[[.x]][1]))) %>%
    rename(time = 1, current = 2, potential = 3)
)
# Summarizing
cap_summary <- cap_df %>%
  group_by(frequency) %>%
  summarize(max(abs(potential)) / max(abs(current))) %>%
  rename(impedance = 2)
```

Now we can graph the frequency vs impedance of the capacitor.
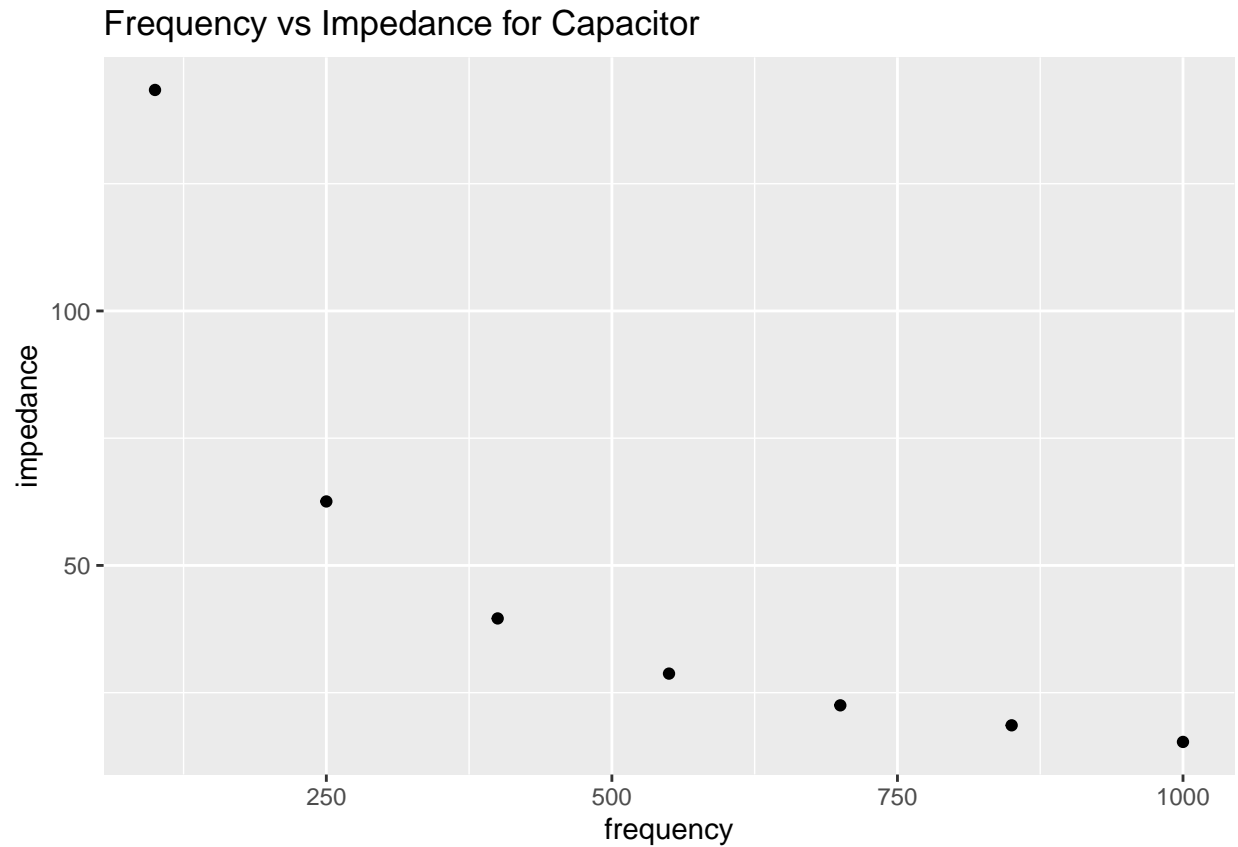
```
# Graphing
ggplot(cap_summary, aes(frequency, impedance)) +
  geom_point() +
  labs(title = "Frequency vs Impedance for Capacitor")
```




This is nonlinear, so we need to linearize our data. We can do this by doing $\frac{1}{\text{impedance}}$.

```
linearized_cap <- cap_summary %>%
  mutate(inv_impedance = 1 / impedance)

ggplot(linearized_cap, aes(frequency, inv_impedance)) +
  geom_point() +
  geom_smooth(method = "lm") +
  labs(title = "Frequency vs 1/impedance for Capacitor")
```
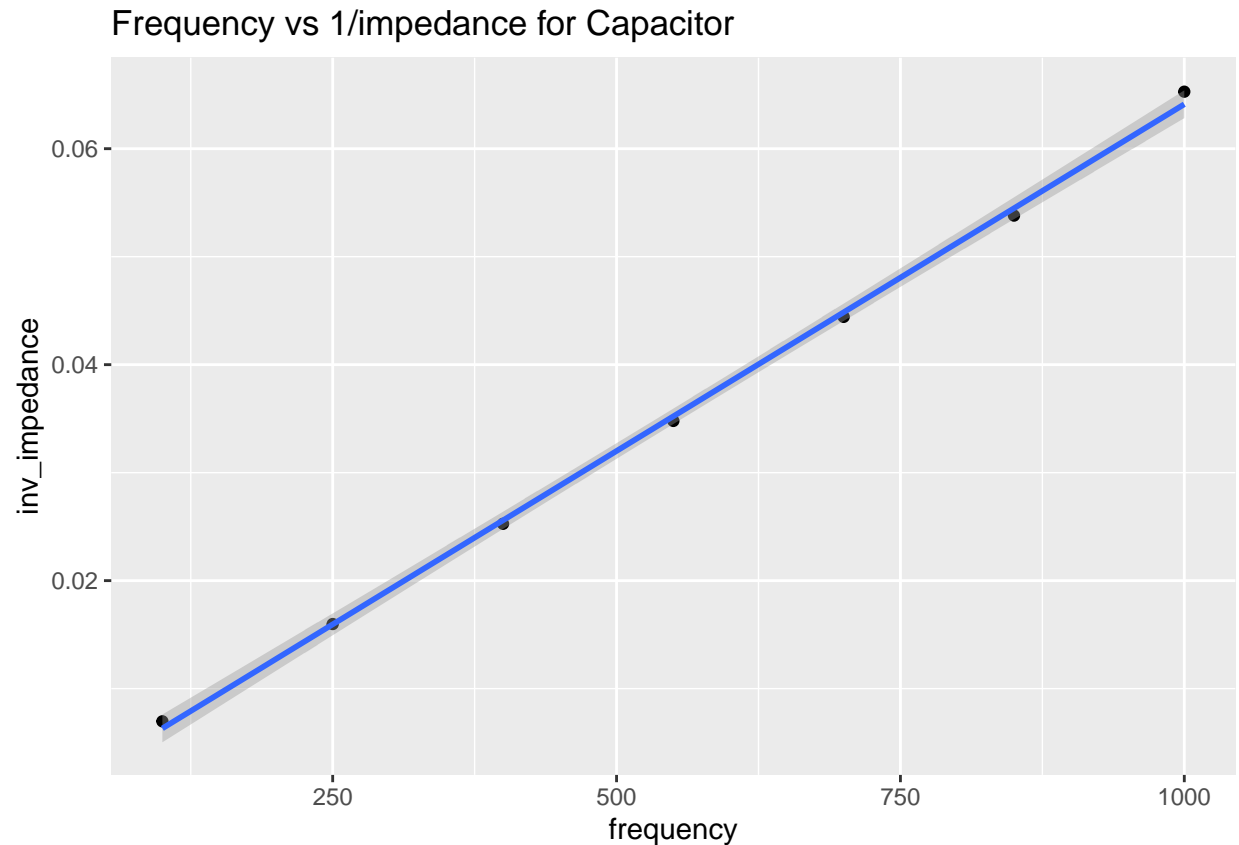
```
## `geom_smooth()` using formula = 'y ~ x'
```



We can fit a linear model to the data.

```
summary(lm(linearized_cap$inv_impedance ~ linearized_cap$frequency))
```

```
##
## Call:
## lm(formula = linearized_cap$inv_impedance ~ linearized_cap$frequency)
##
## Residuals:
```

	1	2	3	4	5	6	7
##	6.553e-04	3.106e-05	-3.205e-04	-4.268e-04	-4.235e-04	-6.780e-04	1.162e-03

```
##
## Coefficients:
```

	Estimate	Std. Error	t value	Pr(> t)
## (Intercept)	-1.052e-04	5.806e-04	-0.181	0.863
## linearized_cap\$frequency	6.422e-05	9.268e-07	69.297	1.19e-08 ***

```
## ---
## Signif. codes:  0 '***' 0.001 '**' 0.01 '*' 0.05 '.' 0.1 ' ' 1
##
## Residual standard error: 0.0007356 on 5 degrees of freedom
## Multiple R-squared:  0.999, Adjusted R-squared:  0.9988
## F-statistic: 4802 on 1 and 5 DF, p-value: 1.185e-08
```

$$\frac{1}{\text{Impedance}} = \text{Frequency} \cdot 0.00006422$$

The units for the slope are:

$$\frac{1}{\text{impedance} \cdot \text{frequency}} \quad (5)$$

$$[s]^2 \quad (6)$$

$$X_c = \frac{1}{2\pi fC} \quad (7)$$

$$\frac{1}{X_c} = 2\pi fC \quad (8)$$

So the slope is equal to Capacitance · 2π.

```
(2 * pi * 10e-6) / 6.422e-05
```

```
## [1] 0.9783845
```

Yes! There is only a small difference between the calculated and empirical values.

Inductor

I expect there be less current at higher frequencies since inductors resist changes in current.


There is an inverse relationship between the frequency and current through a inductor.

```
inductor <- read_csv(here("EECS/frequency_vs_current/input/RLC-inductor.csv"),
                     show_col_types = F)
# Splitting the df into many dfs for every 3 columns
ind_dfs <- map(
  seq(1, ncol(inductor), by = 3),
  ~ inductor[, .x:(.x + 2)]
)
# Getting the frequency as a column
ind_df <- map_df(
  1:length(ind_dfs),
  ~ ind_dfs[[.x]] %>%
    mutate(frequency = parse_number(colnames(ind_dfs[[.x]][1]))) %>%
    rename(time = 1, current = 2, potential = 3)
)
# Summarizing
ind_summary <- ind_df %>%
  group_by(frequency) %>%
  summarize(max(abs(potential)) / max(abs(current))) %>%
  rename(impedance = 2)
```

Now we can graph frequency vs impedance for the inductor.

```
ggplot(ind_summary, aes(frequency, impedance)) +
  geom_point() +
  labs(title = "Frequency vs Impedance of Inductor")
```

Frequency vs Impedance of Inductor

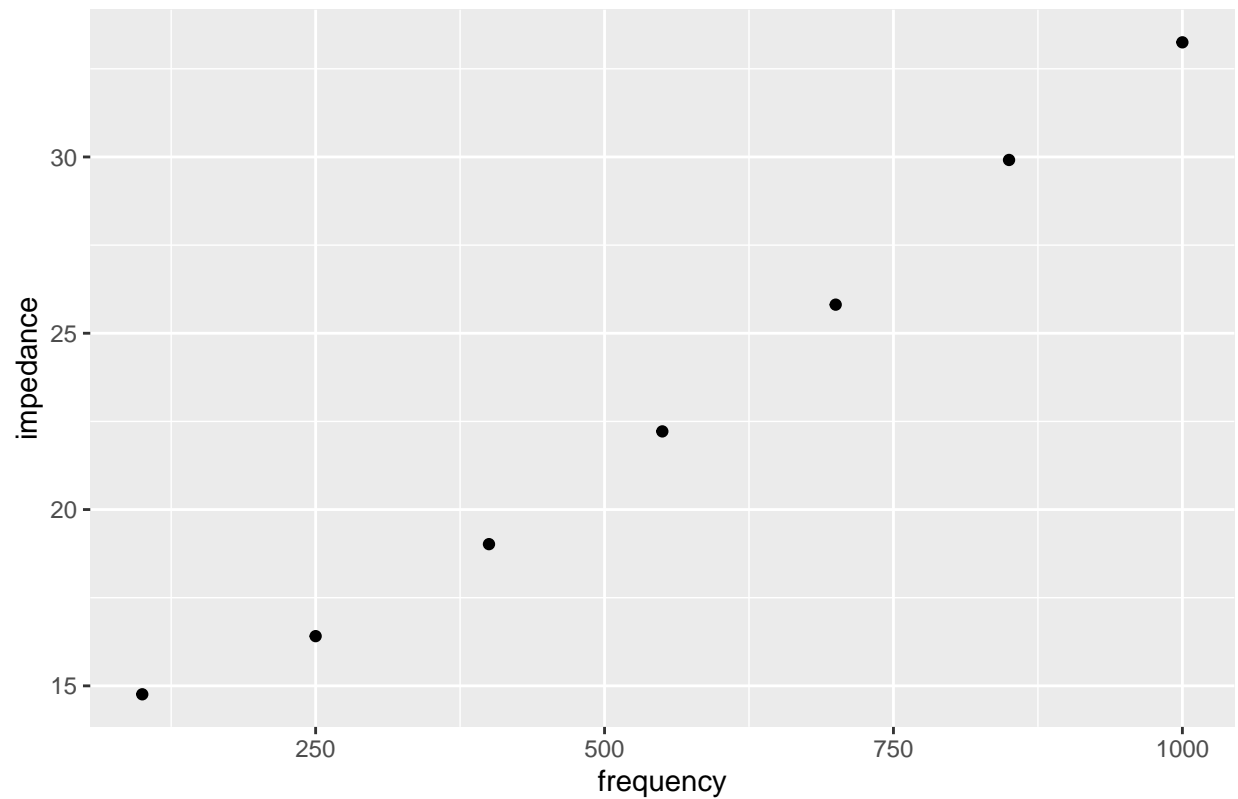

It may appear linear, but it is not!

We need to linearize the data! But I have no idea how to since I thought they were proportional!?!?

```
ggplot(ind_summary, aes(frequency, impedance)) +  
  geom_point() +  
  geom_smooth(method = "lm", se = F) +  
  labs(title = "Linearized Frequency vs Impedance of Inductor")
```

```
## `geom_smooth()` using formula = 'y ~ x'
```

Linearized Frequency vs Impedance of Inductor

